



25AIC11

I SEMESTER BCA (AI) EXAMINATION - NOVEMBER/DECEMBER 2025

SCHEME: Revised CBCS

BCA (Artificial Intelligence)

Computer Fundamentals and Digital Electronics

Time: 03 Hours

Max Marks: 80

Instruction: Answer both Part A & Part B.

PART - A

- | | | |
|--|---------|--|
| 1. Answer ALL questions. | 8x2=16 | |
| a. What is meant by Hardware and Software? | CO1 LL1 | |
| b. What is MSB and LSB? | CO1 LL1 | |
| c. What is the function of compiler? | CO2 LL1 | |
| d. Define Algorithm | CO2 LL1 | |
| e. Define Boolean Algebra | CO3 LL1 | |
| f. Design circuit diagram and truth table for NOT gate | CO3 LL1 | |
| g. What is a Karnaugh Map? | CO4 LL1 | |
| h. What is a combinational circuit? | CO4 LL1 | |

PART - B

Answer any TWO sub questions from each main. 4x16=64

- | | | |
|--|---------|---|
| 2. a) Explain third and fifth generations of computer. | CO1 LL2 | 8 |
| b) Explain in detail the basic organization of a digital computer with a neat diagram. | CO1 LL2 | 8 |
| c) Convert the following: | | |
| i) $(345)_8$ to binary and decimal. | CO1 LL2 | 4 |
| ii) $(1001011)_2$ to decimal and hexadecimal. | CO1 LL2 | 4 |
| d) Discuss in detail computer codes BCD, Gray Code, ASCII and Unicode. | CO1 LL2 | 8 |

25AIC11



3.	a) Explain the different types of softwares.	CO2 LL2	8
	b) Explain the different types of computer languages.	CO2 LL2	8
	c) Explain the different types of computers with respect to their size and speed.	CO2 LL2	8
	d) Write an algorithm and flowchart for the program to calculate the simple interest.	CO2 LL2	8
4.	a) Explain any four Boolean laws.	CO3 LL2	8
	b) What is an IC? Write the circuit diagram and truth table for NAND and NOR gate.	CO3 LL2	8
	c) i) Simplify the equation $\bar{x}\bar{y} + x\bar{y} + xy$ using Boolean Algebra and draw the circuit diagram.	CO3 LL2	4
	ii) Explain basic logic gate and write its truth table.	CO3 LL2	4
	d) Using NAND and NOR gate, construct AND and OR logic gates.	CO3 LL2	8
5.	a) Using K-Map, Simplify the following expression and draw the circuit diagram $F(A,B,C,D) = m1+m2+m4+m5+m9+m11+m12+m13$.	CO4 LL2	8
	b) i) Explain Full-Adder with the circuit diagram.	CO4 LL2	6
	ii) What is Encoder?	CO4 LL2	2
	c) Explain Full Subtractor with circuit diagram and Truth Table.	CO4 LL2	8
	d) Explain the followings:		
	i) Encoder and Decoder.	CO4 LL2	4
	ii) Multiplexer	CO4 LL2	4